

# ELEC 4700 Assignment-3 Monte-Carlo/Finite Difference Method

Assignment 3 - Joanna Abalos 100962263

```
close all
clear
clc

global G;
global C;
global b;

% In this assignment, circuits are modelled and simulated using MNA and
% circuit simulation.

assignment4_1

% By inspection, this is a low pass filter and amplifier. This is known
% because the signal goes through the inductor and a resistor in series
% goes to ground. In DC, the capacitor appears as an open circuit and the
% inductor appears as a short. Reading the output of the inductor will
% result in high frequencies being cutoff.

% The frequency response effectively passes low voltage and cuts off high
% frequencies.

assignment4_2

% Increasing the timestep reduces the accuracy of the model.

assignment4_3

% Adding noise to the circuit does not effect the frequency response
% because high frequency noise is filtered out. The noise is seen on the DC
% response but the general output is close to the circuit without noise.

% Varying values of Cn increases the bandwidth of passing frequencies. At
% higher values of Cn, the circuit becomes overdamped as shown by the peak
% when C = 1. At low values of Cn, the circuit is underdamped as shown by
% the lowest C value. The cutoff varies slightly, but mostly the amplitude
% response of the frequency plot is effected by Cn. This stamp was written
% when I took ELEC4609 last semester.

% If the voltage source was replaced by the transconductance equation, the
% voltage source would need to be converted into the current controlled
% voltage source. The stamp of that is used to implement is as shown
% below:

%      nil -----o+          |-----o nd1
%                               |
%                               /+\
%                               | /  \      Vnd1 - Vnd2 = val*(Vni1 - Vni2)
%                               | \  /
%                               Ivcvs | \  /
```

```

%               V  \-/
%               |
%   ni2  -----o-      |-----o nd2
%
% The nodes across the dependent source are nd1 and nd2 (positive voltage at nd1)
% The independent nodes are ni1 and ni2 (positive voltage at ni1).
%   Vnd1 - Vnd2 = val*(Vni1 - Vni2)

```

Part 1.

C =

Columns 1 through 7

0.2500	-0.2500	0	0	0	0	0
-0.2500	0.2500	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	-0.2000
0	0	0	0	0	0	0

Column 8

0  
0  
0  
0  
0  
0  
0  
0  
0

G =

Columns 1 through 7

1.0000	-1.0000	0	0	0	1.0000	0
-1.0000	1.5000	0	0	0	0	1.0000
0	0	0.1000	0	0	0	-1.0000
0	0	0	10.0000	-10.0000	0	0
0	0	0	-10.0000	10.0010	0	0
1.0000	0	0	0	0	0	0
0	1.0000	-1.0000	0	0	0	0
0	0	-10.0000	1.0000	0	0	0

Column 8

0  
0  
0  
0  
1.0000  
0  
0

0  
0

C after applying random values.  
C =

Columns 1 through 7

0.2351	-0.2351	0	0	0	0	0
-0.2351	0.2351	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	-0.2000
0	0	0	0	0	0	0

Column 8

0  
0  
0  
0  
0  
0  
0  
0  
0

Part 3.  
Updated C matrix:  
C =

Columns 1 through 7

0.2500	-0.2500	0	0	0	0	0
-0.2500	0.2500	0	0	0	0	0
0	0	0.0000	-0.0000	0	0	0
0	0	-0.0000	0.0000	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0

Columns 8 through 10

0	0	0
0	0	0
0	0	0
0	0	0
0	0	0
0	0	0
0	0	0
-0.2000	0	0

0 0 0  
0 0 0













